

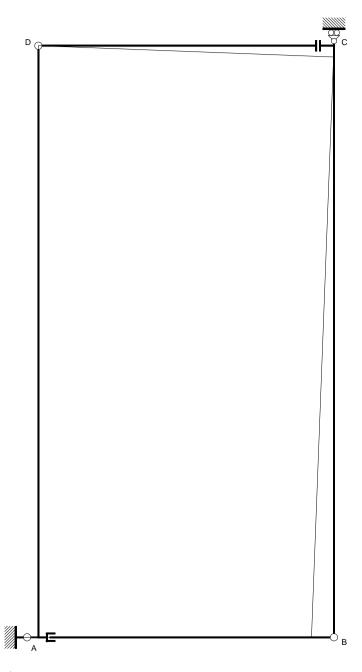


Soluzione del sistema
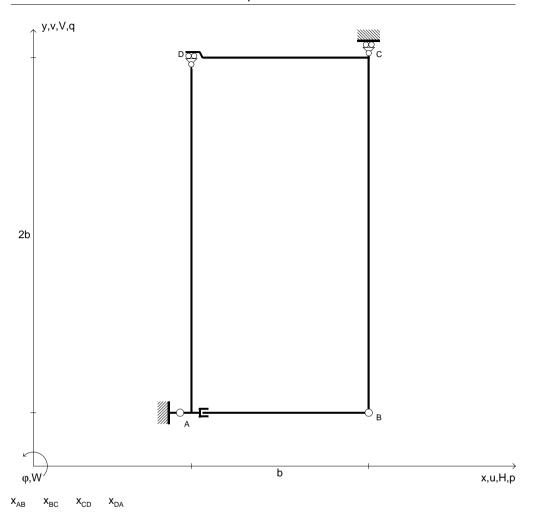
$$\begin{bmatrix} \phi_A b \\ u_{AB} \\ v_{CD} \\ \phi_{DC} b \end{bmatrix} = \begin{bmatrix} \phi_{DC} b \\ 0 \\ 2 \\ -1 \\ 1 \end{bmatrix}$$




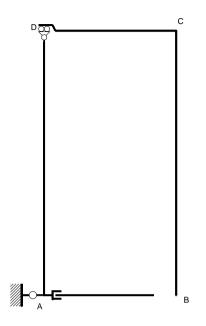





$$\begin{bmatrix} \phi_A b & u_{AB} & \phi_{DC} b & u_{DA} \end{bmatrix} \\ v_C & \begin{bmatrix} 1 & 0 & 1 & 0 \\ 0 & 1 & -2 & -1 \\ v_{BA} & 0 & 0 & -1 & 0 \end{bmatrix}$$
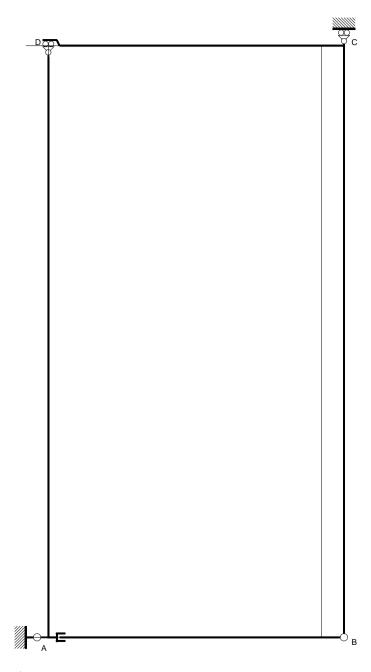
$$\begin{bmatrix} \phi_A b \\ u_{AB} \\ \phi_{DC} b \\ u_{DA} \end{bmatrix} = \begin{bmatrix} u_{DA} \\ 0 \\ 1 \\ 0 \\ 1 \end{bmatrix}$$



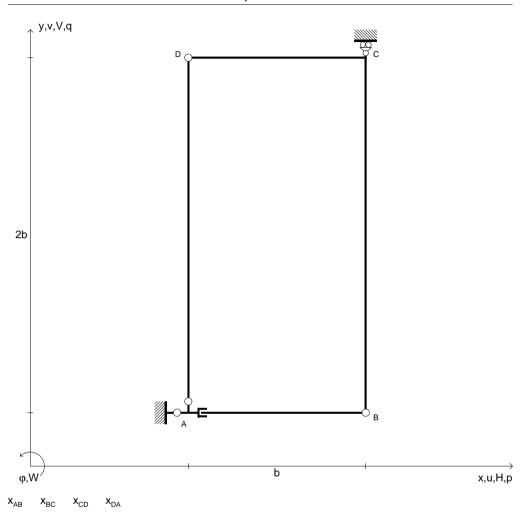


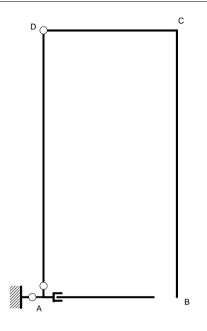



Soluzione del sistema

$$\begin{bmatrix} \phi_A b \\ u_{AB} \\ \phi_{AD} b \\ \phi_{DC} b \end{bmatrix} = \begin{bmatrix} \phi_{DC} b \\ 0 \\ 2 \\ -1 \\ 1 \end{bmatrix}$$


Es.N.037

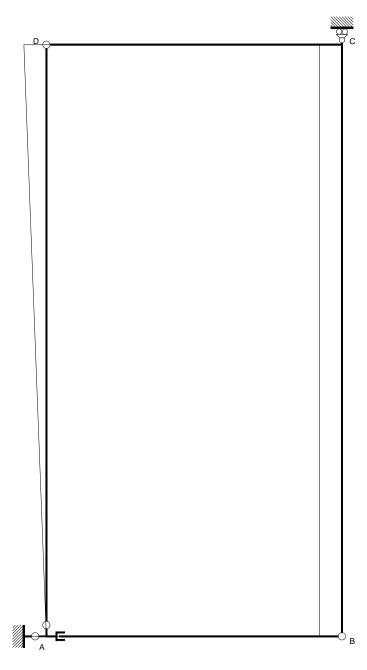


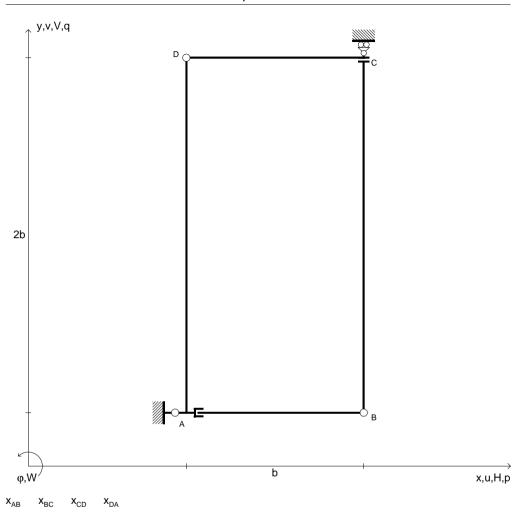


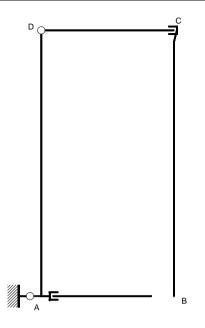

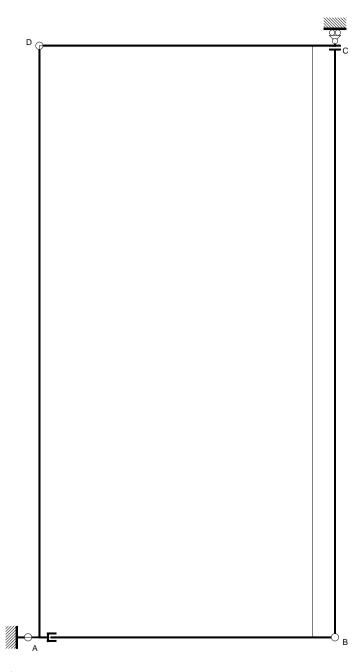
$$\begin{bmatrix} \phi_A b \\ u_{AB} \\ \phi_{DC} b \\ u_{CB} \end{bmatrix} = \begin{bmatrix} u_{CB} \\ 0 \\ 1 \\ 0 \\ 1 \end{bmatrix}$$




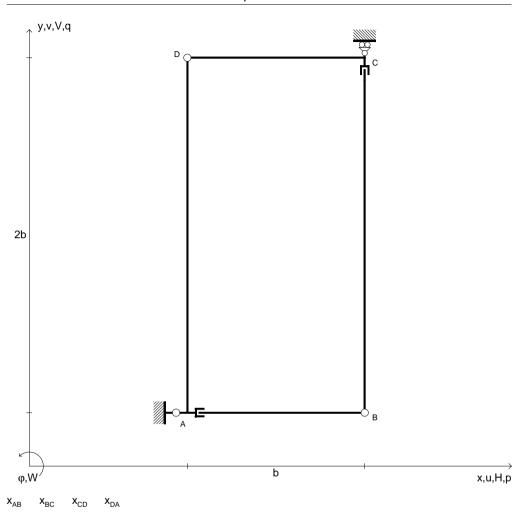


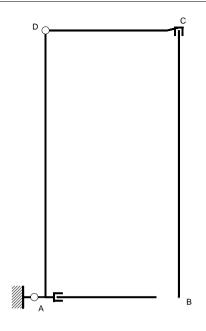
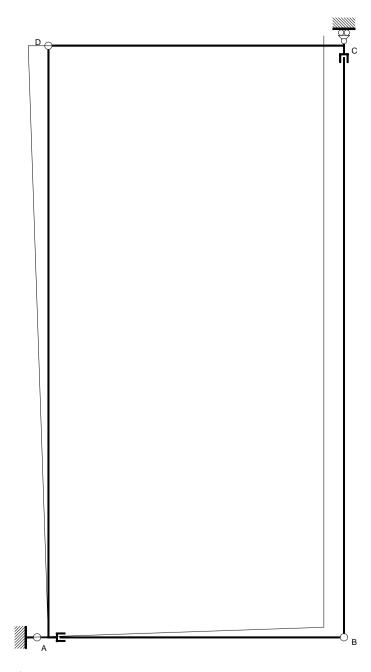
$$\begin{bmatrix} \phi_A b \\ u_{AB} \\ \phi_{DA} b \\ v_{CB} \end{bmatrix} = \begin{bmatrix} v_{CB} \\ 1 \\ -2 \\ -1 \\ 1 \end{bmatrix}$$



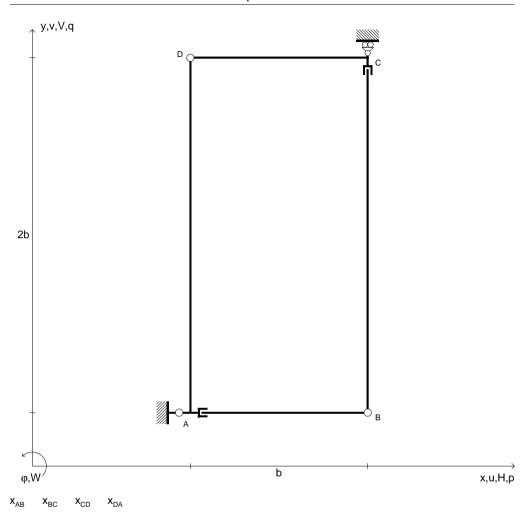

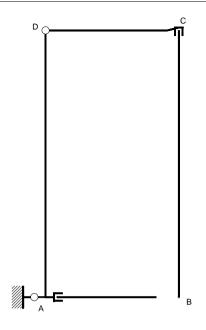

$$\begin{bmatrix} \phi_A b \\ u_{AB} \\ \phi_{DC} b \\ v_{CB} \end{bmatrix} = \begin{bmatrix} v_{CB} \\ 1 \\ -2 \\ -1 \\ 1 \end{bmatrix}$$



